

CS250 Computer Architecture

A Single-Cycle MIPS Processor

A single-cycle MIPS processor

- As previously discussed, an instruction set architecture is an *interface* that defines the hardware operations that are available to software.
- Any instruction set can be implemented in many different ways. Over the next few classes we'll compare two important implementations.
 - In a basic **single-cycle implementation** all operations take the same amount of time—a single cycle.
 - In a **pipelined implementation**, a processor can overlap the execution of several instructions, potentially leading to big performance gains.

Single-cycle implementation

- In this lecture, we will describe the implementation a simple MIPS-based instruction set supporting just the following operations.

Arithmetic:	add	sub	and	or	slt
Data Transfer:	lw	sw			
Control:	beq				

- We use MIPS because it is significantly easier to implement than x86.
- Today we'll build a **single-cycle implementation** of this instruction set.
 - All instructions will execute in the same amount of time; this will determine the clock cycle time for our performance equations.
 - We'll explain the datapath first, and then make the control unit.



August 18, 2016

A single-cycle MIPS processor

3

Memories

- It's easier to use a **Harvard architecture** at first, with programs and data stored in *separate* memories.
- To fetch instructions and read & write words, we need these memories to be 32-bits wide (buses are represented by dark lines here), so these are $2^{30} \times 32$ memories. (We will ignore byte addressability for the moment.)
- Blue lines represent control signals. **MemRead** and **MemWrite** should be set to 1 if the **data memory** is to be read or written respectively, and 0 otherwise.
 - When a control signal does something when it is set to 1, we call it **active high** (vs. active low) because 1 is usually a higher voltage than 0.
- For today, we will assume you cannot write to the **instruction memory**.
 - Pretend it's already loaded with a program, which doesn't change while it's running.

 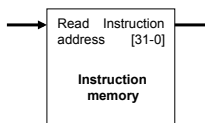


August 18, 2016

A single-cycle MIPS processor

4

Instruction fetching

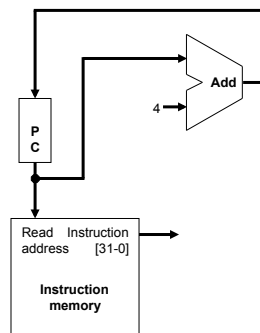- The CPU is always in an infinite loop, fetching instructions from memory and executing them.
- The **program counter** or **PC** register holds the address of the current instruction.
- MIPS instructions are each four bytes long, so the PC should be incremented by four to read the next instruction in sequence.



August 18, 2016

A single-cycle MIPS processor

5

Encoding R-type instructions

- A few weeks ago, we saw encodings of MIPS instructions as 32-bit values.
- Register-to-register arithmetic instructions use the **R-type** format.
 - op** is the instruction opcode, and **func** specifies a particular arithmetic operation (see the back of the textbook).
 - rs**, **rt** and **rd** are source and destination registers.

op	rs	rt	rd	shamt	func
6 bits	5 bits	5 bits	5 bits	5 bits	6 bits

- An example instruction and its encoding:

add \$s4, \$t1, \$t2

000000	01001	01010	10100	00000	1000000
--------	-------	-------	-------	-------	---------


August 18, 2016

A single-cycle MIPS processor

6

Registers and ALUs

 - R-type instructions must access registers and an ALU.
- Our **register file** stores thirty-two 32-bit values.
 - Each register specifier is 5 bits long.
 - You can read from two registers at a time.
 - **RegWrite** is 1 if a register should be written.
- Here's a simple **ALU** with five operations, selected by a 3-bit control signal **ALUOp**.




ALUOp	Function
000	and
001	or
010	add
110	subtract
111	slt

August 18, 2016

A single-cycle MIPS processor

Executing an R-type instruction

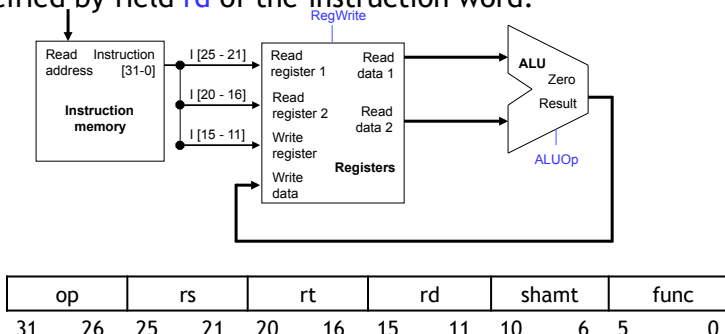1. Read an instruction from the instruction memory.
2. The source registers, specified by instruction fields **rs** and **rt**, should be read from the register file.
3. The ALU performs the desired operation.
4. Its result is stored in the destination register, which is specified by field **rd** of the instruction word.



August 18, 2016

A single-cycle MIPS processor

8

Encoding I-type instructions

- The lw, sw and beq instructions all use the **I-type** encoding.
 - rt** is the *destination* for lw, but a *source* for beq and sw.
 - address** is a 16-bit signed constant.

op	rs	rt	address
6 bits	5 bits	5 bits	16 bits

- Two example instructions:

lw \$t0, -4(\$sp) 100011 11101 01000 1111 1111 1111 1100

sw \$a0, 16(\$sp) 101011 11101 00100 0000 0000 0001 0000


August 18, 2016

A single-cycle MIPS processor

9

Accessing data memory

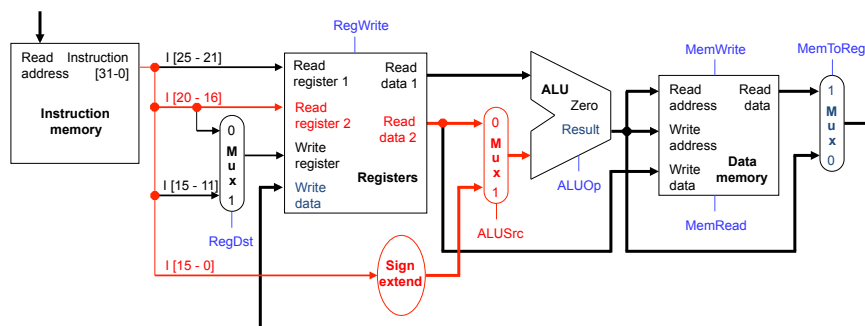- For an instruction like lw \$t0, -4(\$sp), the base register \$sp is added to the *sign-extended* constant to get a data memory address.
- This means the ALU must accept *either* a register operand for arithmetic instructions, *or* a sign-extended immediate operand for lw and sw.
- We'll add a multiplexer, controlled by ALUSrc, to select either a register operand (0) or a constant operand (1).




August 18, 2016

A single-cycle MIPS processor

10

MemToReg

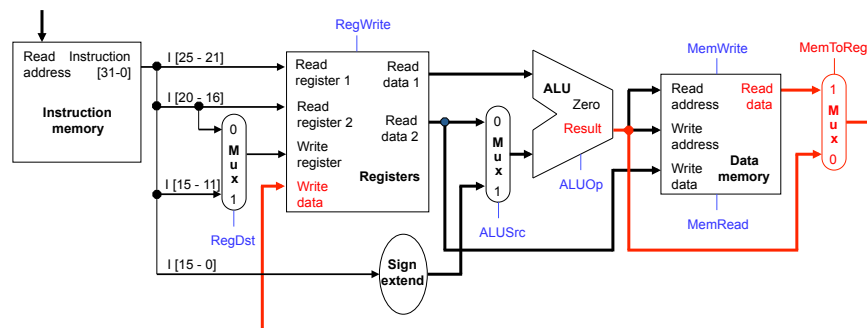- The register file's "Write data" input has a similar problem. It must be able to store *either* the ALU output of R-type instructions, *or* the data memory output for lw.
- We add a mux, controlled by **MemToReg**, to select between saving the ALU result (0) or the data memory output (1) to the registers.



August 18, 2016

A single-cycle MIPS processor

11


RegDst

- A final annoyance is the destination register of lw is in **rt** instead of **rd**.

op	rs	rt	address
----	----	----	---------

lw \$rt, address(\$rs)

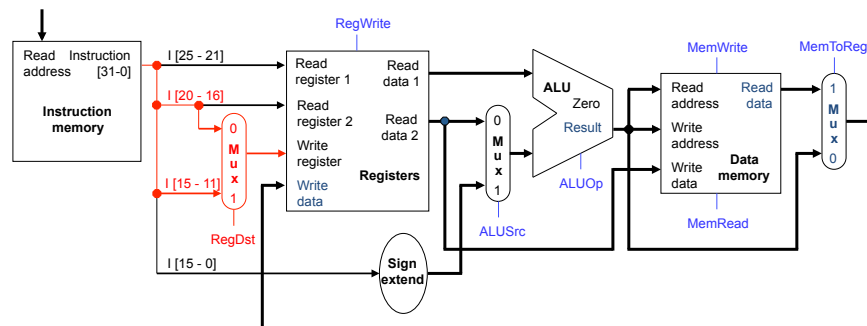- We'll add one more mux, controlled by **RegDst**, to select the destination register from either instruction field **rt** (0) or field **rd** (1).



August 18, 2016

A single-cycle MIPS processor

12

Branches

- For branch instructions, the constant is not an address but an *instruction offset* from the current program counter to the desired address.

```

    beq    $a1, $0, L
    add    $v1, $v0, $0
    add    $v1, $v1, $v1
    j      Somewhere
L:        add    $v1, $v0, $v0
  
```

- The target address L is three *instructions* past the `beq`, so the encoding of the branch instruction has 0000 0000 0000 0011 for the address field.

000100	00001	00000	0000 0000 0000 0011
op	rs	rt	address

- Instructions are four bytes long, so the actual memory offset is 12 bytes.

August 18, 2016

A single-cycle MIPS processor

13

The steps in executing a beq

1. Fetch the instruction, like `beq $a1, $0, offset`, from memory.
2. Read the source registers, `$a1` and `$0`, from the register file.
3. Compare the values by subtracting them in the ALU.
4. If the subtraction result is 0, the source operands were equal and the PC should be loaded with the target address, $PC + 4 + (\text{offset} \times 4)$.
5. Otherwise the branch should not be taken, and the PC should just be incremented to $PC + 4$ to fetch the next instruction sequentially.


August 18, 2016

A single-cycle MIPS processor

14

Branching hardware

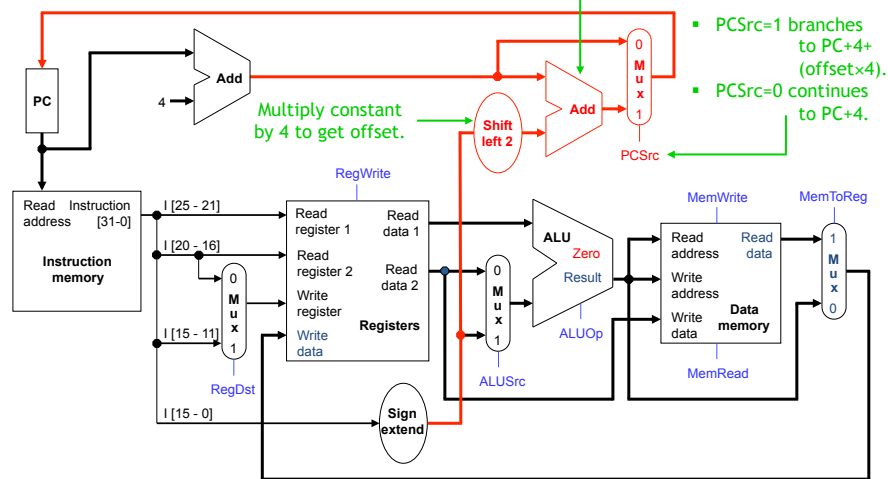We need a second adder, since the ALU is already doing subtraction for the beq.




August 18, 2016

A single-cycle MIPS processor

15

The final datapath

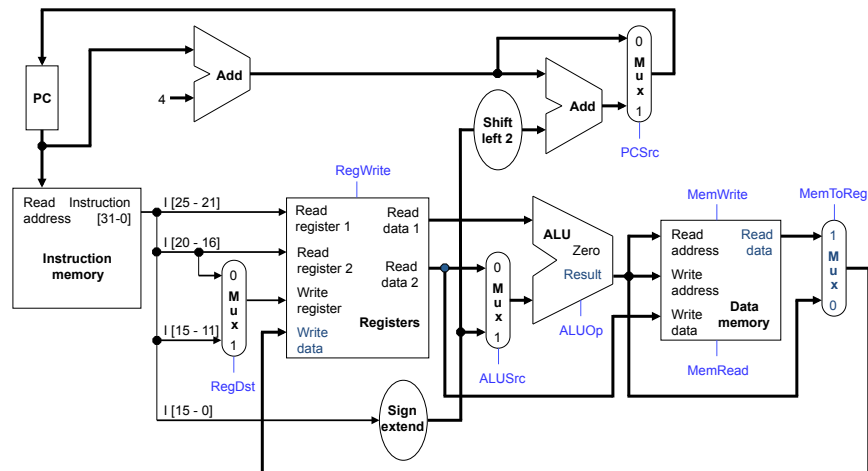

August 18, 2016

A single-cycle MIPS processor

16

Control



- The **control unit** is responsible for setting all the control signals so that each instruction is executed properly.
 - The control unit's input is the 32-bit instruction word.
 - The outputs are values for the blue control signals in the datapath.
- Most of the signals can be generated from the instruction opcode alone, and not the entire 32-bit word.
- To illustrate the relevant control signals, we will show the route that is taken through the datapath by R-type, lw, sw and beq instructions.


August 18, 2016

A single-cycle MIPS processor

17

R-type instruction path

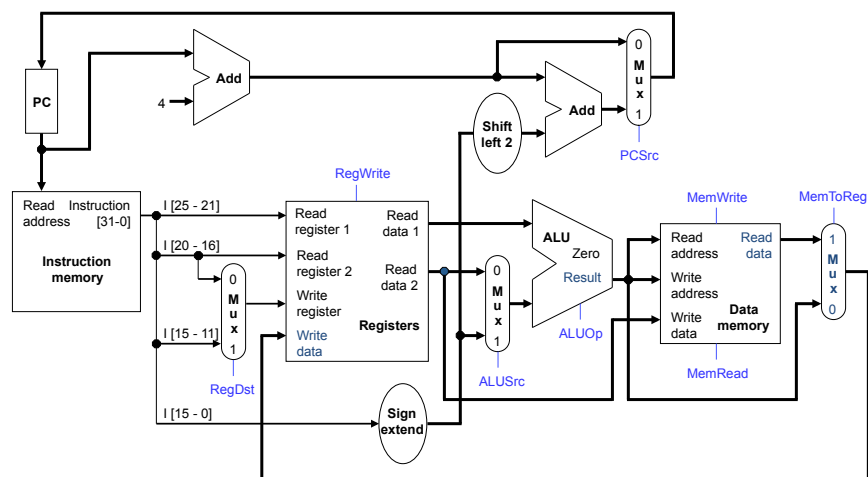- The R-type instructions include **add**, **sub**, **and**, **or**, and **slt**.
- The **ALUOp** is determined by the instruction's "func" field.




August 18, 2016

A single-cycle MIPS processor

18

lw instruction path

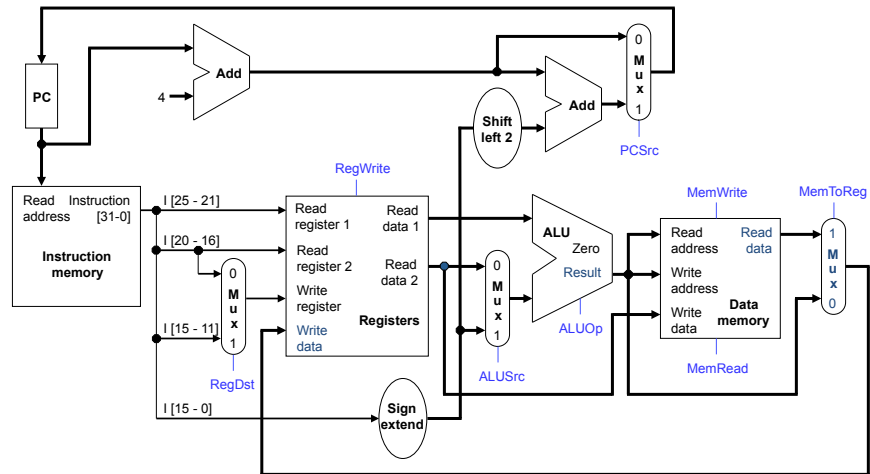- An example load instruction is `lw $t0, -4($sp)`.
- The **ALUOp** must be 010 (add), to compute the effective address.




August 18, 2016

A single-cycle MIPS processor

19

sw instruction path

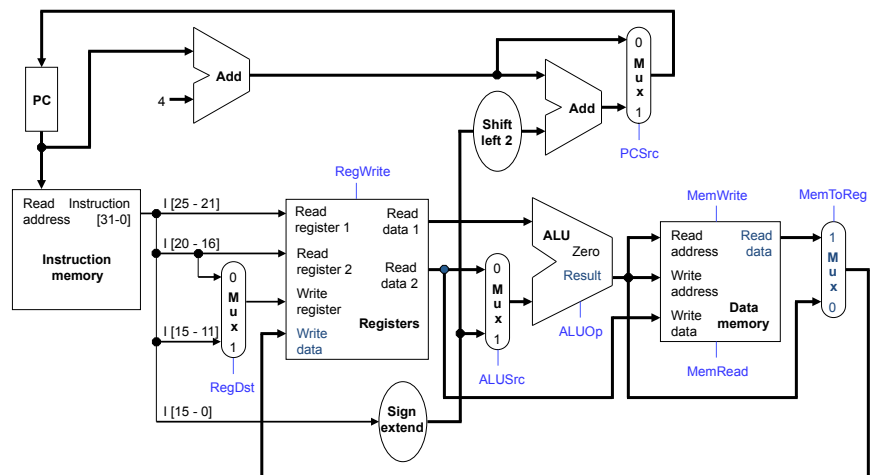- An example store instruction is `sw $a0, 16($sp)`.
- The **ALUOp** must be 010 (add), again to compute the effective address.




August 18, 2016

A single-cycle MIPS processor

20

beq instruction path

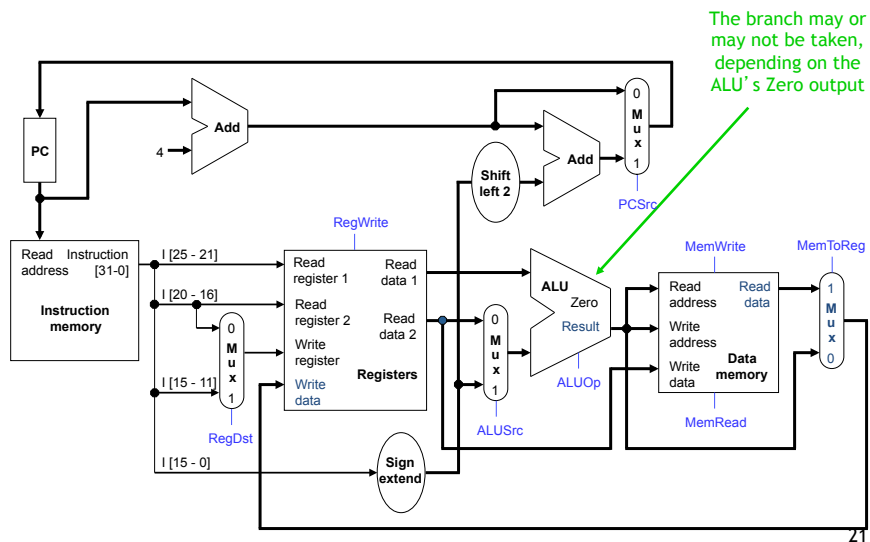- One sample branch instruction is `beq $at, $0, offset`.
- The **ALUOp** is 110 (subtract), to test for equality.




Control signal table

Operation	RegDst	RegWrite	ALUSrc	ALUOp	MemWrite	MemRead	MemToReg
add	1	1	0	010	0	0	0
sub	1	1	0	110	0	0	0
and	1	1	0	000	0	0	0
or	1	1	0	001	0	0	0
slt	1	1	0	111	0	0	0
lw	0	1	1	010	0	1	1
sw	X	0	1	010	1	0	X
beq	X	0	0	110	0	0	X

- `sw` and `beq` are the only instructions that do not write any registers.
- `lw` and `sw` are the only instructions that use the constant field. They also depend on the ALU to compute the effective memory address.
- **ALUOp** for R-type instructions depends on the instructions' func field.
- The PCSrc control signal (not listed) should be set if the instruction is `beq` and the ALU's Zero output is true.

Generating control signals

- The control unit needs 13 bits of inputs.
 - Six bits make up the instruction's opcode.
 - Six bits come from the instruction's func field.
 - It also needs the Zero output of the ALU.
- The control unit generates 10 bits of output, corresponding to the signals mentioned on the previous page.
- You can build the actual circuit by using big K-maps, big Boolean algebra, or big circuit design programs.
- The textbook presents a slightly different control unit.

 

August 18, 2016

23

Summary

- A **datapath** contains all the functional units and connections necessary to implement an instruction set architecture.
 - For our **single-cycle implementation**, we use two separate memories, an ALU, some extra adders, and lots of multiplexers.
 - MIPS is a 32-bit machine, so most of the buses are 32-bits wide.
- The **control unit** tells the datapath what to do, based on the instruction that's currently being executed.
 - Our processor has ten **control signals** that regulate the datapath.
 - The control signals can be generated by a combinational circuit with the instruction's 32-bit binary encoding as input.

August 18, 2016

A single-cycle MIPS processor

24